

# Resistance & Resistivity

## Question paper 3

<b>Level</b>	International A Level
<b>Subject</b>	Physics
<b>Exam Board</b>	CIE
<b>Topic</b>	Current of Electricity
<b>Sub Topic</b>	Resistance & Resistivity
<b>Paper Type</b>	Theory
<b>Booklet</b>	Question paper 3

**Time Allowed:** 51 minutes

**Score:** /42

**Percentage:** /100

A*	A	B	C	D	E	U
>85%	'77.5%	70%	62.5%	57.5%	45%	<45%

- 1 A battery of electromotive force (e.m.f.) 12V and internal resistance  $r$  is connected in series to two resistors, each of constant resistance  $X$ , as shown in Fig. 5.1.

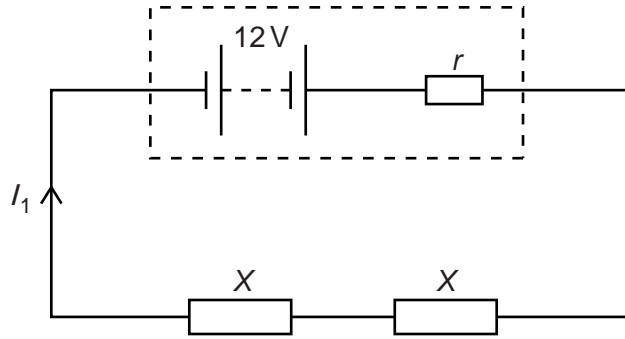


Fig. 5.1

The current  $I_1$  supplied by the battery is 1.2 A.

The same battery is now connected to the same two resistors in parallel, as shown in Fig. 5.2.

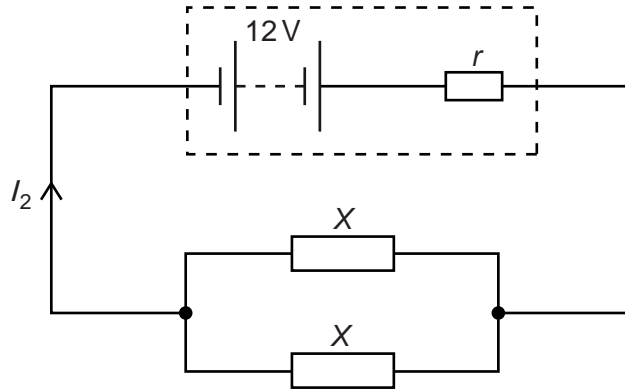


Fig. 5.2

The current  $I_2$  supplied by the battery is 3.0 A.

- (a) (i) Show that the combined resistance of the two resistors, each of resistance  $X$ , is four times greater in Fig. 5.1 than in Fig. 5.2.

[2]

- (ii) Explain why  $I_2$  is not four times greater than  $I_1$ .

.....  
 .....  
 ..... [2]

(iii) Using Kirchhoff's second law, state equations, in terms of e.m.f., current,  $X$  and  $r$ , for

1. the circuit of Fig. 5.1,

.....

2. the circuit of Fig. 5.2.

.....

[2]

(iv) Use the equations in (iii) to calculate the resistance  $X$ .

$$X = \text{.....} \Omega \text{ [1]}$$

(b) Calculate the ratio

$$\frac{\text{power transformed in one resistor of resistance } X \text{ in Fig. 5.1}}{\text{power transformed in one resistor of resistance } X \text{ in Fig. 5.2}}$$

$$\text{ratio} = \text{.....} \text{ [2]}$$

(c) The resistors in Fig. 5.1 and Fig. 5.2 are replaced by identical 12V filament lamps.

Explain why the resistance of each lamp, when connected in series, is not the same as the resistance of each lamp when connected in parallel.

.....

.....

.....

..... [2]

- 2 Two resistors A and B have resistances  $R_1$  and  $R_2$  respectively. The resistors are connected in series with a battery, as shown in Fig. 6.1.

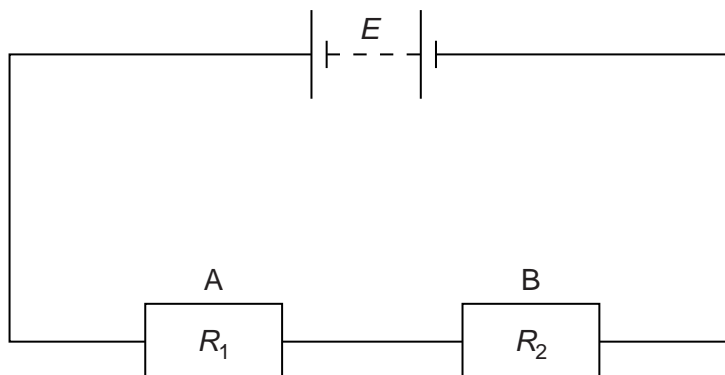


Fig. 6.1

The battery has electromotive force (e.m.f.)  $E$  and zero internal resistance.

- (a) State the energy transformation that occurs in

(i) the battery,

.....  
 ..... [1]

(ii) the resistors.

.....  
 ..... [1]

- (b) The current in the circuit is  $I$ .

State the rate of energy transformation in

(i) the battery,

..... [1]

(ii) the resistor A.

..... [1]

(c) The resistors are made from metal wires. Data for the resistors are given in Fig. 6.2.

resistor	A	B
resistivity of metal	$\rho$	$\rho/2$
length of wire	$l$	$l$
diameter of wire	$d$	$2d$

**Fig. 6.2**

Use information from Fig. 6.2 to determine the ratio

$$\frac{\text{power dissipated in A}}{\text{power dissipated in B}}$$

ratio = ..... [3]

(d) The resistors A and B are connected in parallel across the same battery of e.m.f.  $E$ . Determine the ratio

$$\frac{\text{power dissipated in A}}{\text{power dissipated in B}}$$

ratio = ..... [2]

3 (a) Define electrical *resistance*.

.....  
..... [1]

(b) A circuit is set up to measure the resistance  $R$  of a metal wire. The potential difference (p.d.)  $V$  across the wire and the current  $I$  in the wire are to be measured.

(i) Draw a circuit diagram of the apparatus that could be used to make these measurements.

[3]

(ii) Readings for p.d.  $V$  and the corresponding current  $I$  are obtained. These are shown in Fig. 2.1.

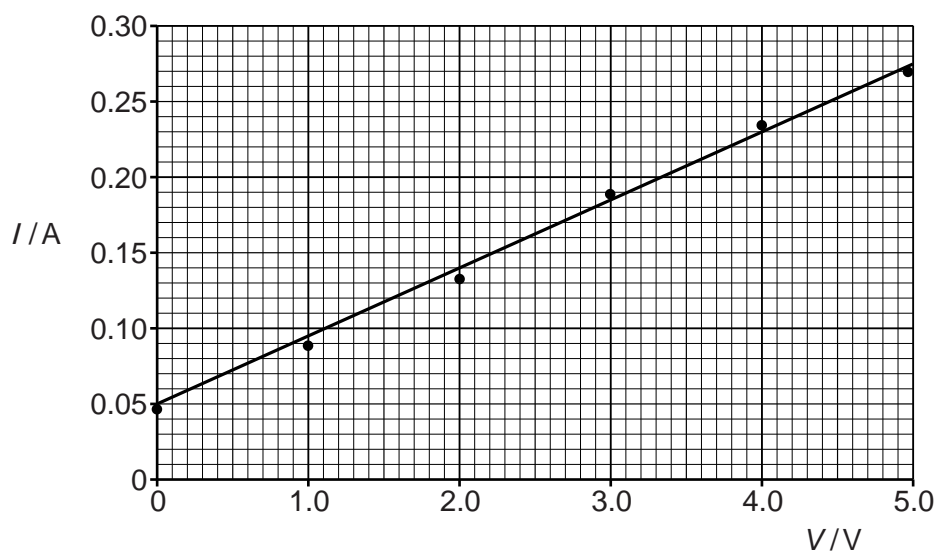


Fig. 2.1

Explain how Fig. 2.1 indicates that the readings are subject to

1. a systematic uncertainty,

.....  
..... [1]

2. random uncertainties.

.....  
..... [1]

(iii) Use data from Fig. 2.1 to determine  $R$ . Explain your working.

$R = \dots\dots\dots \Omega$  [3]

(c) In another experiment, a value of  $R$  is determined from the following data:

Current  $I = 0.64 \pm 0.01$  A and p.d.  $V = 6.8 \pm 0.1$  V.

Calculate the value of  $R$ , together with its uncertainty. Give your answer to an appropriate number of significant figures.

$R = \dots\dots\dots \pm \dots\dots\dots \Omega$  [3]

4 Measurements made for a sample of metal wire are shown in Fig. 1.1.

quantity	measurement	uncertainty
length	1750 mm	$\pm 3$ mm
diameter	0.38 mm	$\pm 0.01$ mm
resistance	$7.5 \Omega$	$\pm 0.2 \Omega$

Fig. 1.1

(a) State the appropriate instruments used to make each of these measurements.

(i) length

..... [1]

(ii) diameter

..... [1]

(iii) resistance

..... [1]

(b) (i) Show that the resistivity of the metal is calculated to be  $4.86 \times 10^{-7} \Omega \text{ m}$ .

[2]

(ii) Calculate the uncertainty in the resistivity.

uncertainty =  $\pm$  .....  $\Omega \text{ m}$  [4]



- (c) Use the answers in (b) to express the resistivity with its uncertainty to the appropriate number of significant figures.

resistivity = .....  $\pm$  .....  $\Omega \text{ m}$  [1]